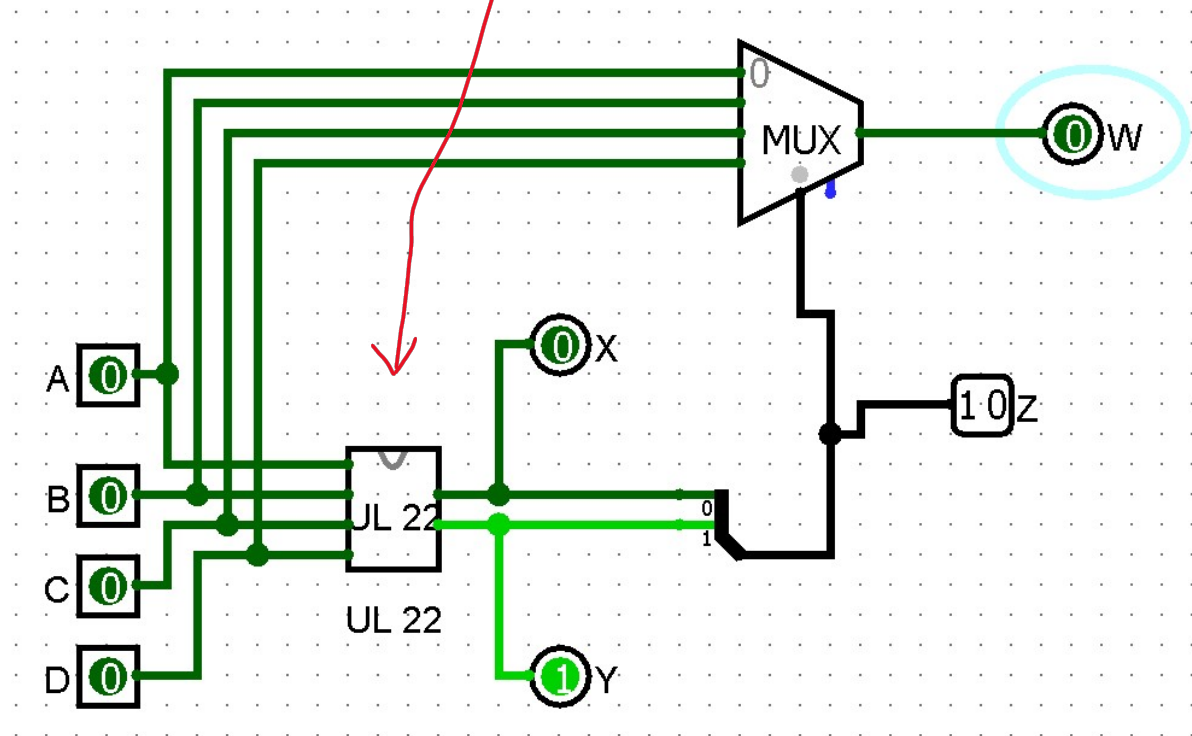


Ülesanne 23

1. Koostada skeem

NB Skeemis kasutatakse UL 22 skeemi



Lisainfo:

Selection: UL 22	
Facing	East
Label	
Label Location	North
Label Font	SansSerif Plain 12
Circuit Name	UL 22
Shared Label	UL 22
Shared Label Facing	North
Shared Label Font	SansSerif Plain 12

Selection: Splitter	
Facing	West
Fan Out	2
Bit Width In	2
Appearance	Right-handed
Bit 0	0 (Top)
Bit 1	1 (Bottom)

Selection: Multiplexer	
Facing	East
Select Location	Bottom/Left
Select Bits	2
Data Bits	1
Disabled Output	Floating
Include Enable?	Yes

2. Vasta küsimustele

<https://moodle.tktk.ee/mod/scorm/view.php?id=131147>